

Посреди моста

A1

$\mathcal{E}_0 =$

$r_0 =$

A2

$I_{AB} =$

A3

$P_{\text{н.э}} =$

A4**B1**

$I_C(t) =$

B2

$Q_{\text{н.э}} =$

B3

$\tau =$

B4

$I_C(t) =$

B5

$Q_{\text{н.э}} =$